
Electronic Music Interactions


(EMI)
GROUP #1

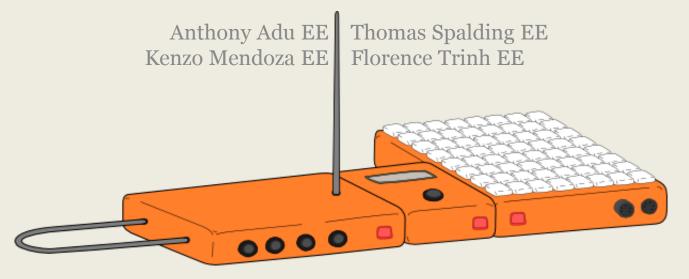Modern and alternative interactions with music devices




Goals & Objectives

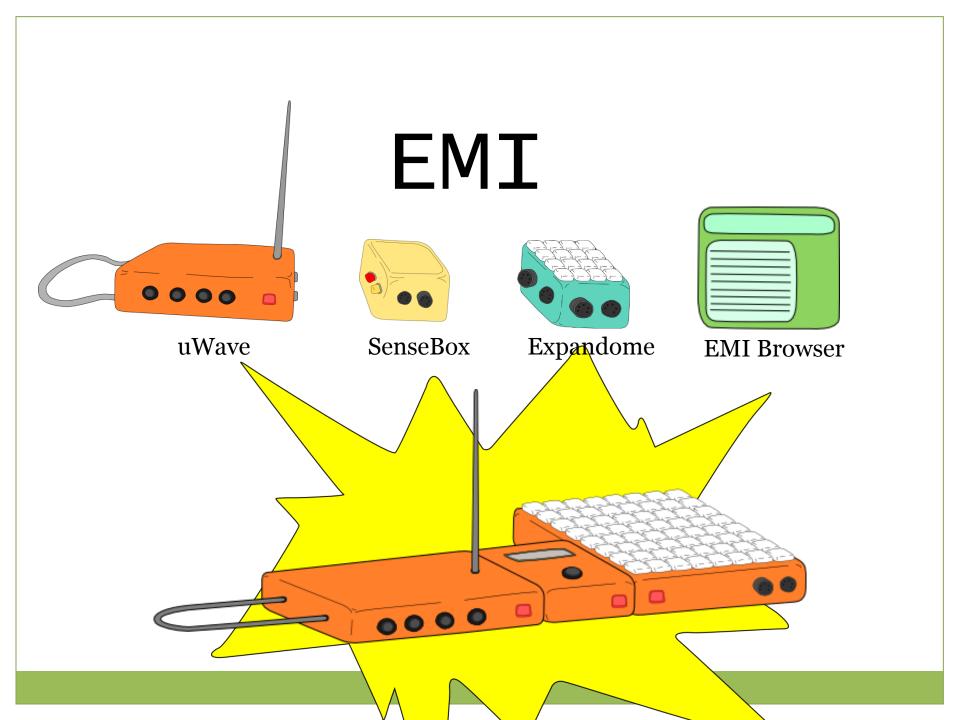- Create a customizable and interactive musical device.
- Integrating a classically analog instrument with a modern digital experience.
- Implement a direct-feedback environment to facilitate learning experience



Prior Similar Work



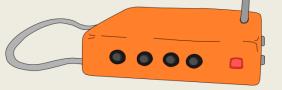

uWave



Robert Moog Innovator

PITCH-TO-MIDI TRACKER



SenseBox



Hobbyist


ARDUINOME MIDI CONTROLLER






Stephen Hobley Jordan Hochenbaum & Owen Vallis Researchers

uWave Theremin

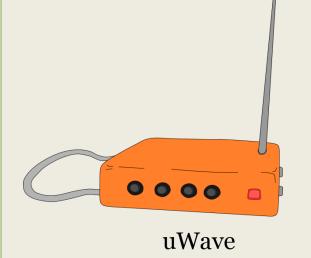



 



Expandome




EMI Browser

uWave Theremin Specifications

- Operate with a power supply of ±12V
- Two coil antennas to control pitch frequency and volume
- Output a max voltage of o.8Vrms
- Oscillators operate at frequencies close to resonance frequency of their respective antennas circuits (260 & 450 kHz)
- Output sufficient analog signal(o to 3 kHz) for digital conversion

Theremin - Design Approach

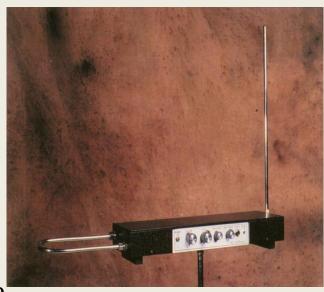- The basic elements of a Theremin are
 - Oscillators for pitch control
 - Oscillator for volume control
 - Mixer and Detector
 - Audio amplification
- Robert Moog EM Theremin
 - Known for the Moog Synthesizer
 - Recreated the original Theremin in 1948
 - Released the electronic Theremin DIY guide in 1996




Antenna Circuits


Pitch Antenna

- o 18" Vertical
- Creates a resonance frequency of 260 kHz

Volume Antenna

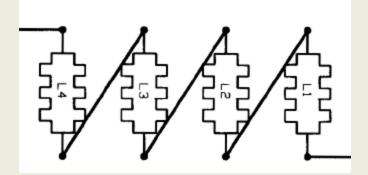- Looped and 9" horizontal
- Creates a resonance frequency of 450 kHz




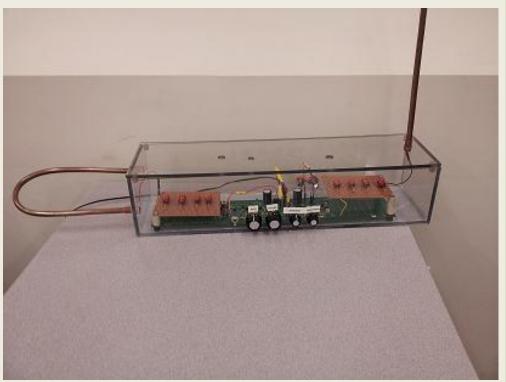


Antenna Circuits



ACTUAL ANTENNA CIRCUIT

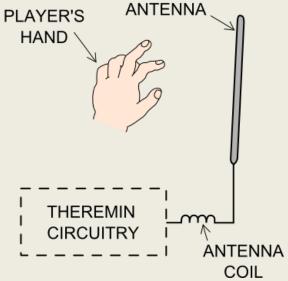

EQUIVALENT CIRCUIT

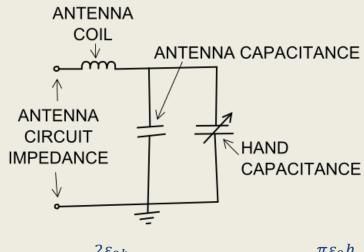

$$C_A = \frac{2\varepsilon_{0h}}{\log \frac{2h}{d} - k}$$
 $C_{hand} = \frac{\pi\varepsilon_0 h}{10 \log \frac{4x}{d}}$

 $C_A = Antenna\ Capacitance$ $C_{hand} = Imposed\ hand\ capacitance$ $h = antenna\ height(m)$ $d = antenna\ diameter(m)$ $\varepsilon_0 = 8.85\ x\ 10^{-12} Fm^{-1}$ $x = hand\ distance\ from\ theremin\ (m)$ k is a constant that depends on how far above ground the antenna is


Pitch Oscillators




General frequency equation

•
$$f_{osc} = \frac{1}{2\pi\sqrt{L(C_2 + C_A + C_{hand})}}$$

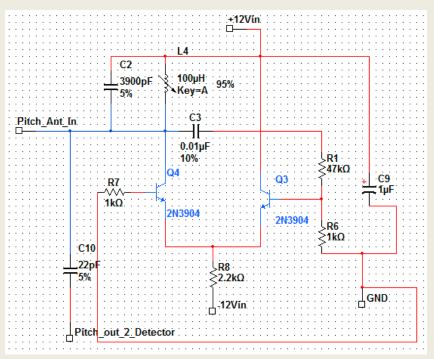- FPO -> 285 kHz
- VPO -> 282 to 285 kHz
- Frequency manipulation
 - Active impedance circuit (FPO)
 - Pitch Antenna (VPO)



Tuning Circuit

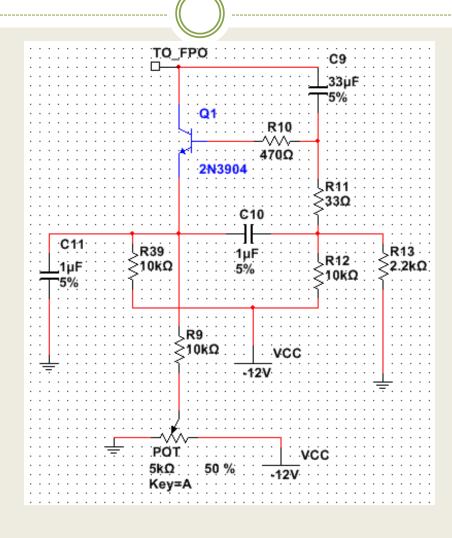


Frequency Detection

- Heterodyning: Method of mixing two signals to create one signal with two frequency components.
- $V_{mix} = \frac{A}{2} [\cos(2\pi f_1 2\pi f_2)t \cos(2\pi f_1 + 2\pi f_2)]$
- Output from detector


$$V_{out} = \frac{A}{2}\cos(2\pi f_1 - 2\pi f_2)t$$

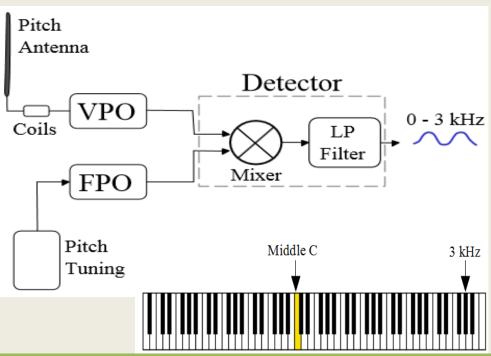Where f_1 = FPO frequency & f_2 = VPO frequency




Volume Oscillator

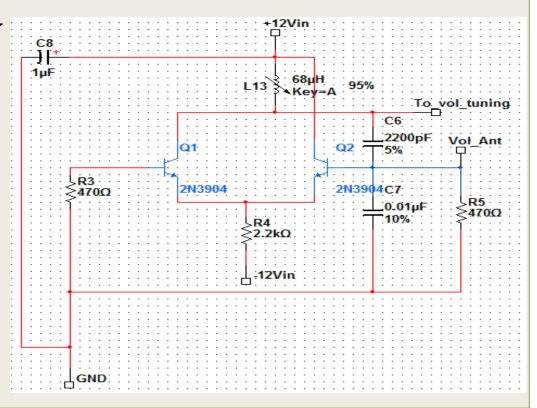- Operates at higher frequency of 432 kHz
- Creates DC voltage used by the VCA
- Adjustable Frequency
 - Volume Tuning




Design cont'd

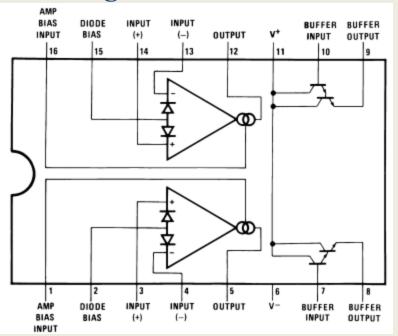- Voltage Controlled Amplifier (VCA)
 - LM13700 Dual Operational Transconductance Amplifier
 - Amplifies pitch signal from detector
 - Max audio output voltage of o.8 Vrms



SenseBox

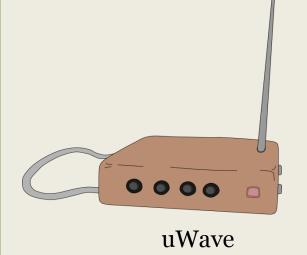







Expandome




EMI Browser

SenseBox Specifications


- Operate with a power supply of +5V
- Receive analog signal from uWave Theremin (o.8 VRMS) and convert to MIDI data
- 4 Mode operation Pitch, Control, ARP1 & ARP2
- 1 LCD that will display but not limited to: current mode operation, note name based on the current pitch, volume value, incoming MIDI note number from a MIDI device.
- 8 LEDs to display visual aid for user (volume and pitch accuracy)

Microprocessor - Atmega328


Parameter	Arduino Uno
Chip	Atmega328p
Analog input	6 pins
Flash Memory	32KB
RAM Memory	2KB
Communication Protocols	Serial
Bits Per Second	Adjustable
(Baud)	(32,250 bit
	per second
	for MIDI
	protocol)

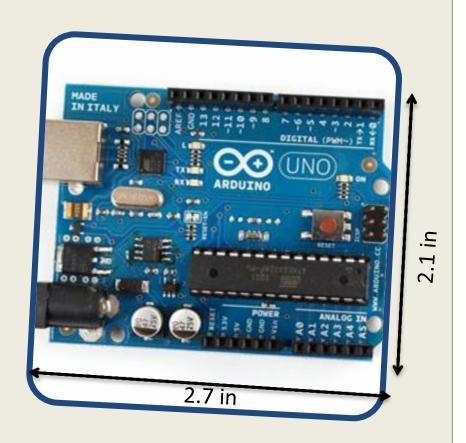


Block Diagram of SenseBox

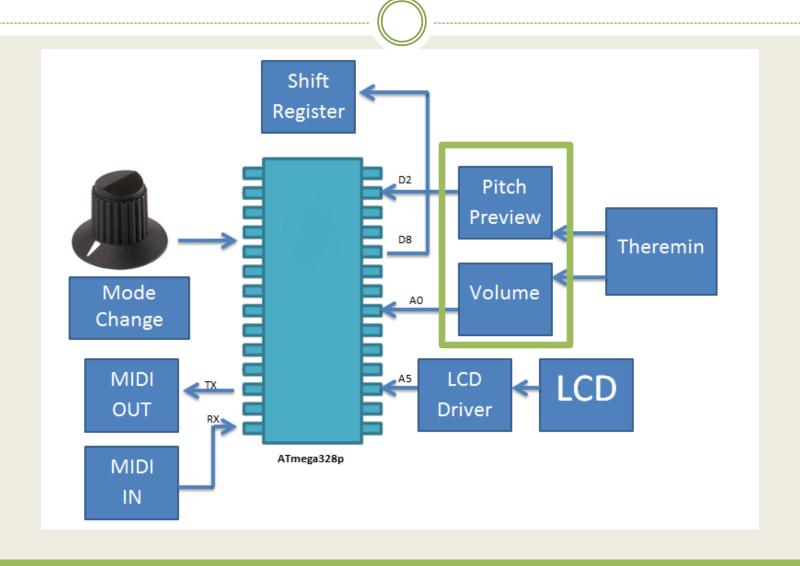


SenseBox - Pitch and Volume Data

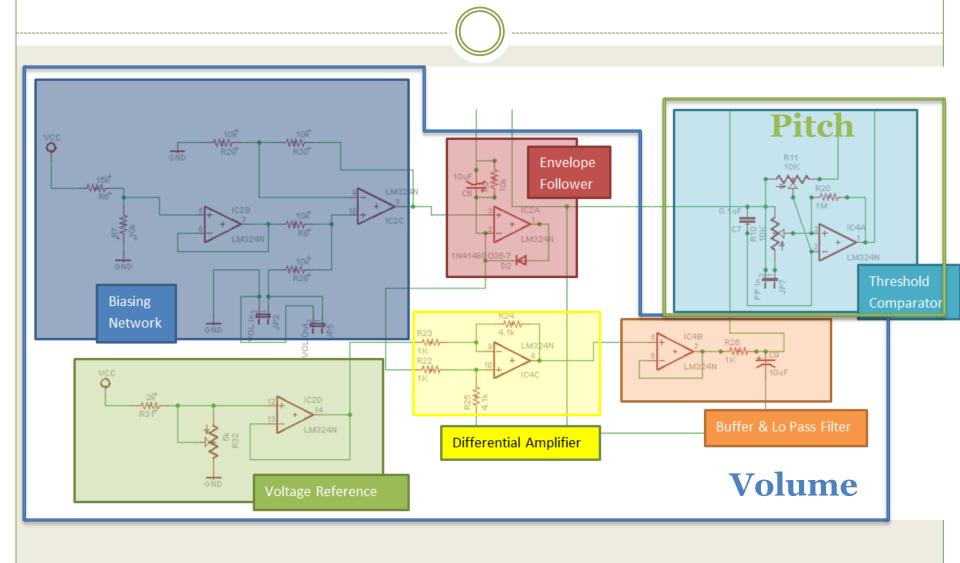


Biasing Network

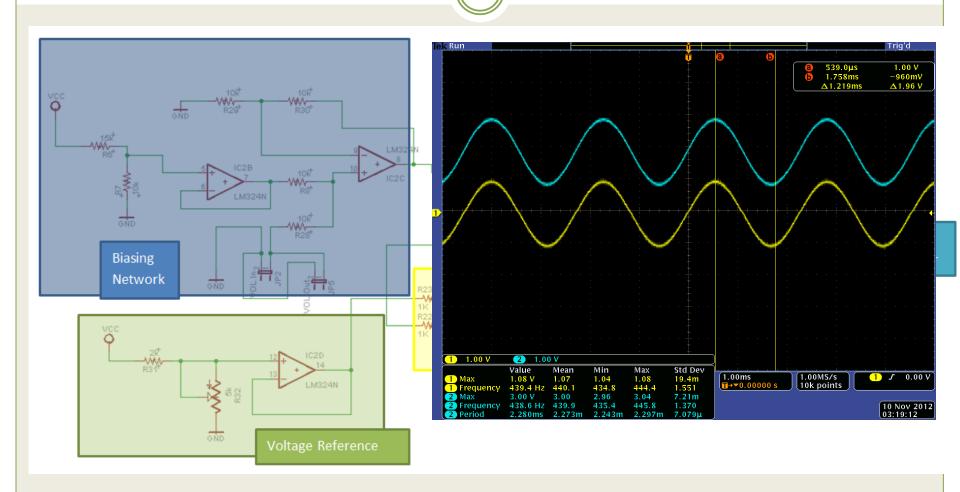

Envelope Follower

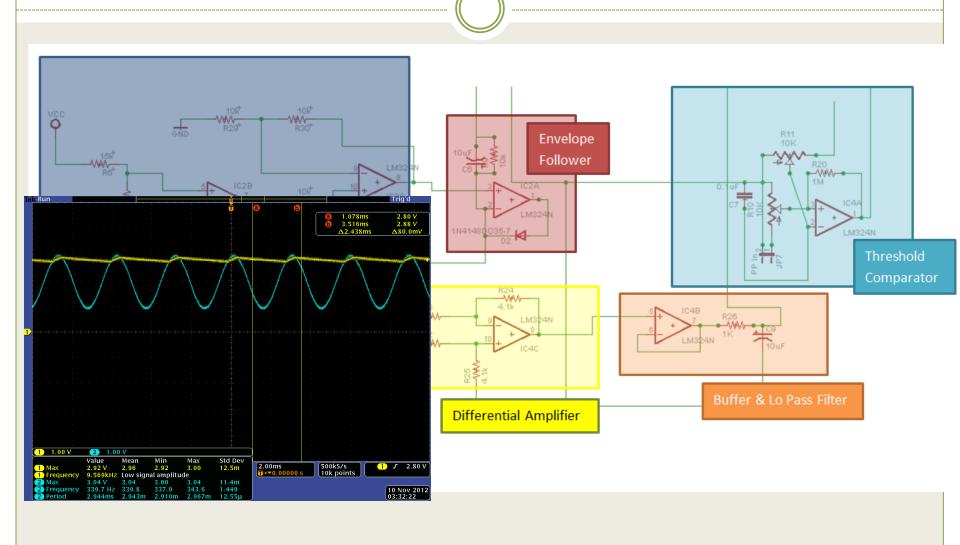


Differential Amplifier (Output Volume)

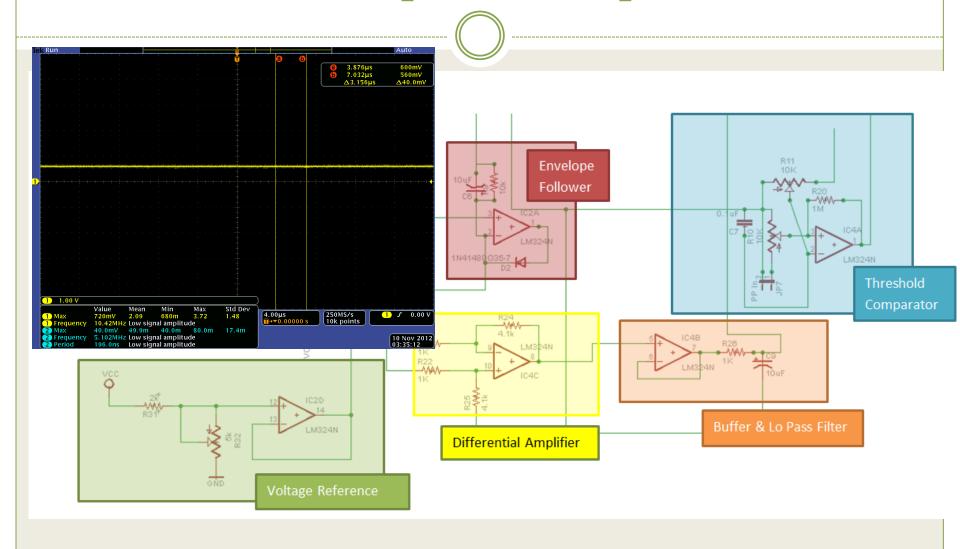

Threshold Comparator



Block Diagram of SenseBox

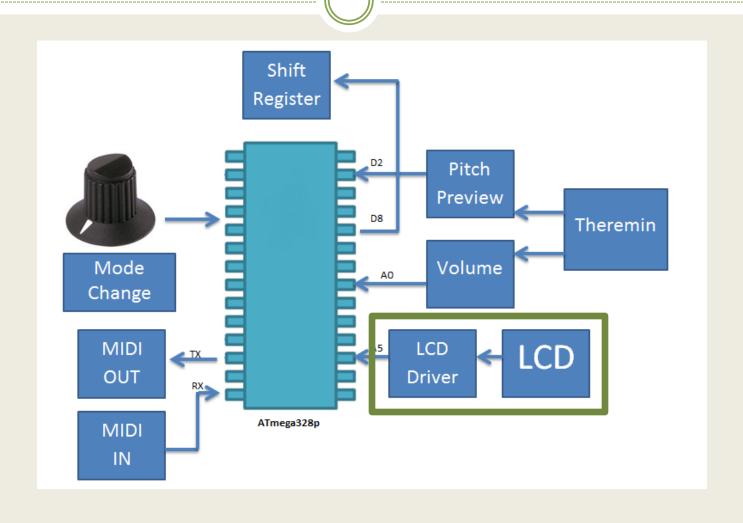

LCD Panel / LCD 117 Driver


Parameter	20 X 4 LCD	
Communication	Serial	
Color	White LED on blue screen	
Operating Voltage	5V	
Backlighting	Included 3	.6 in



- Eliminate the number of pins from 14 to 3 pins
- Ground, Serial Data and 5 V supply
- Contains a microprocessor
 - Allows the programmer to use built-in functions
 - Backlighting
 - Serial print of LCD screen
 - Clear Screen
 - × Many more...

2.7 in


Block Diagram of SenseBox

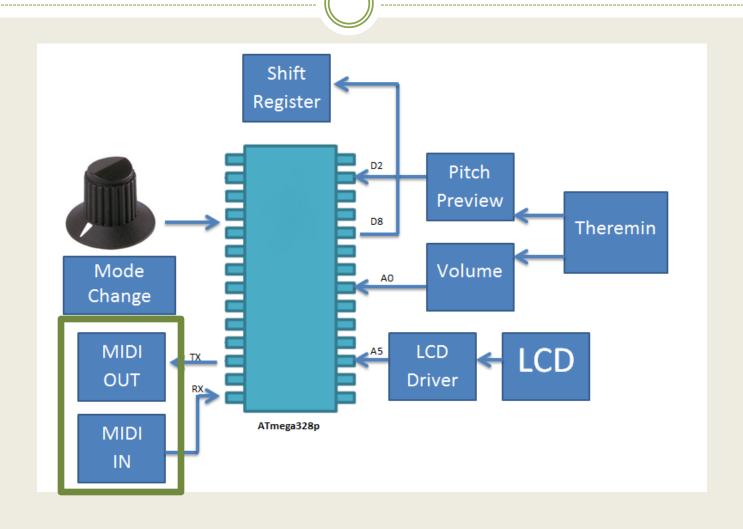

MIDI OUT Schematic

MIDI OUT Pinout	
PIN	Description
1	Not Connected
2	Grounded
3	Not Connected
4	Current Sink
5	Current Source

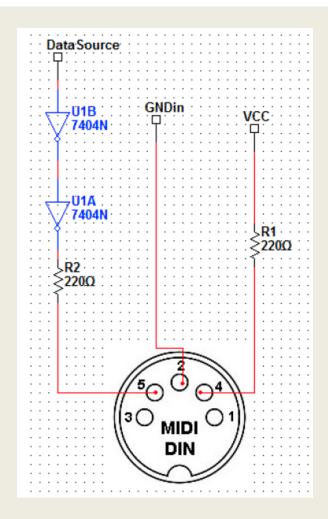
Copyright 1985 MIDI Manufactures Association




MIDI IN Schematic

MIDI IN Pinout		
PIN	Description	
1	Not Connected	
2	Not Connected	
3	Not Connected	
4	Current Source	
5	Current Sink	

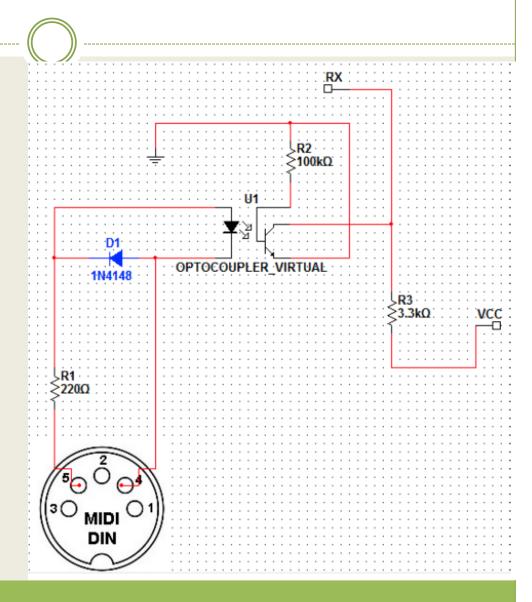Copyright 1985 MIDI Manufactures Association



Block Diagram of SenseBox

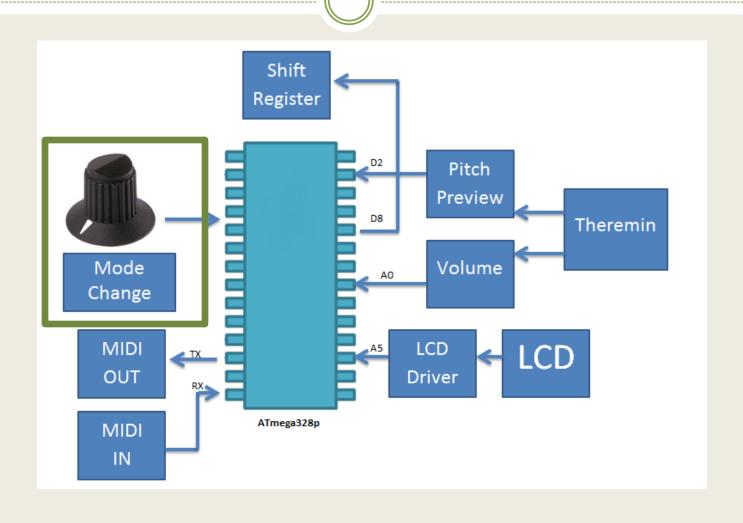


Mode Operation Explanation


Function	Description
Pitch	Track the frequency and volume from the uWave Theremin and display and output the corresponding MIDI data
Control	Output a control data based on the theremin's pitch magnitude
ARP1*	Read an input from MIDI keyboard and arpegiate based on how many keys are pressed
ARP2*	Read an input from MIDI keyboard and arpegiate around the collection of notes that are held on the keyboard


^{*}In order to use these operations, a MIDI keyboard must be connected to the SenseBox

Block Diagram of SenseBox

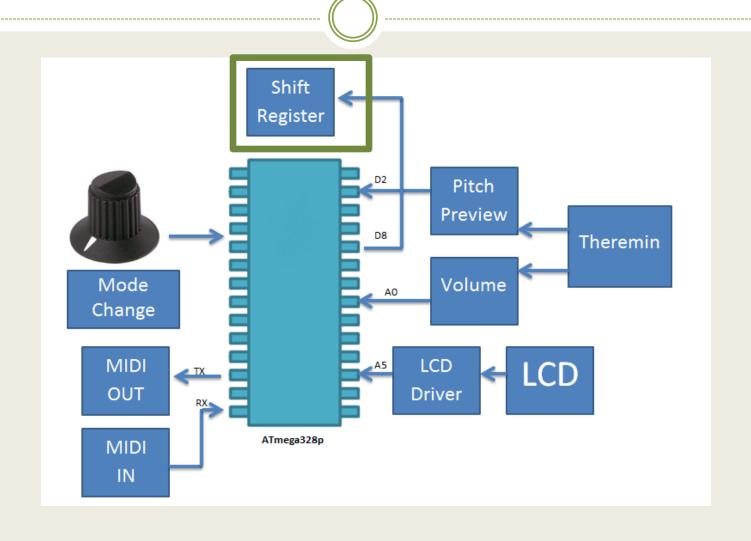


Pitch and Volume Accuracy

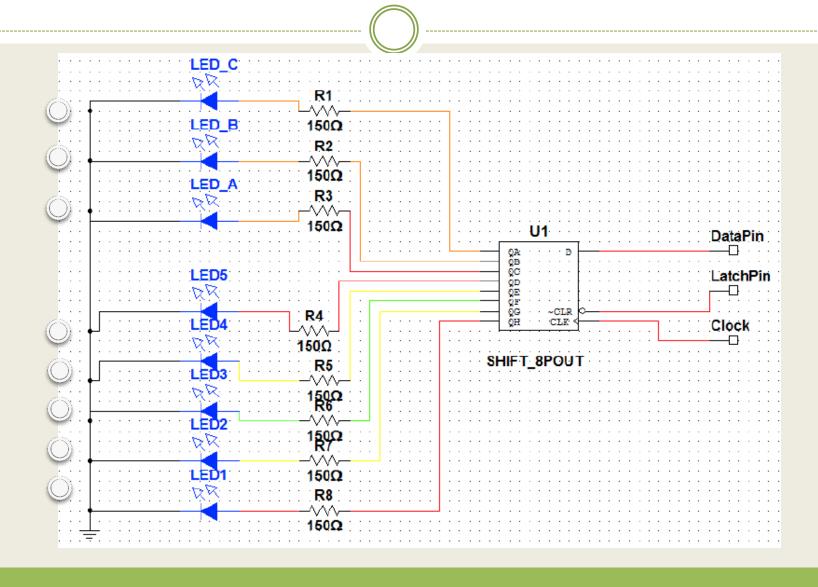

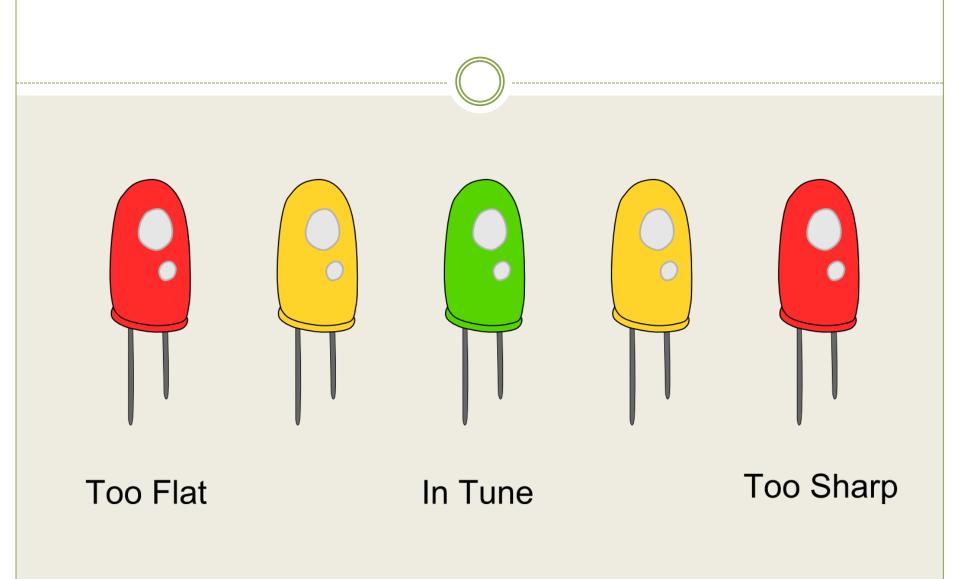

Expandome

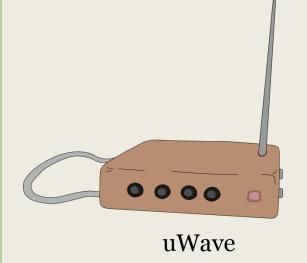







Expandome



EMI Browser


Expandome Specifications


- *n* x *m* pushbutton grid, per device (4x4, 4x8, or 8x8)
- OSC/MIDI controller capabilities
- Device recognition and interaction with any standard VST, and via Pure Data is capable of anything from intensive audio abstraction to a simple control pad
- All Expandome firmware embedded on ATmega microprocessor
- Operate with 5V with max current draw of 500mA

Expandome – Design Approach

Primary Elements

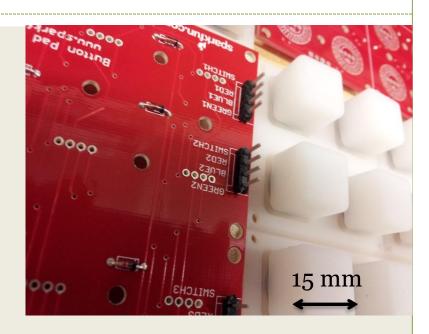- Silicon Pushbuttons
- Buttonpad PCB, and Diodes
- Shift Registers
- USB port connectors
- Integrated barebones
 Arduino clone



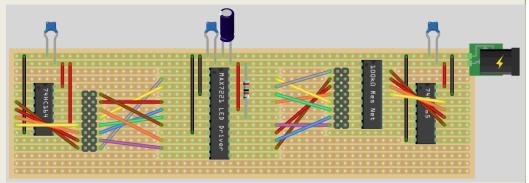


Stripboard representation of Unsped board made by monome.org user Josephiah

Microprocessor—Atmega328

Parameter	Atmega328
Flash	32Kbytes
CPU	8-bit AVR
Max I/O pins	23
SRAM Memory	2KB
Expandome Device	4x4, 4x8 or 8x8
Image	
	1.4 inches



Expandome Block Diagram

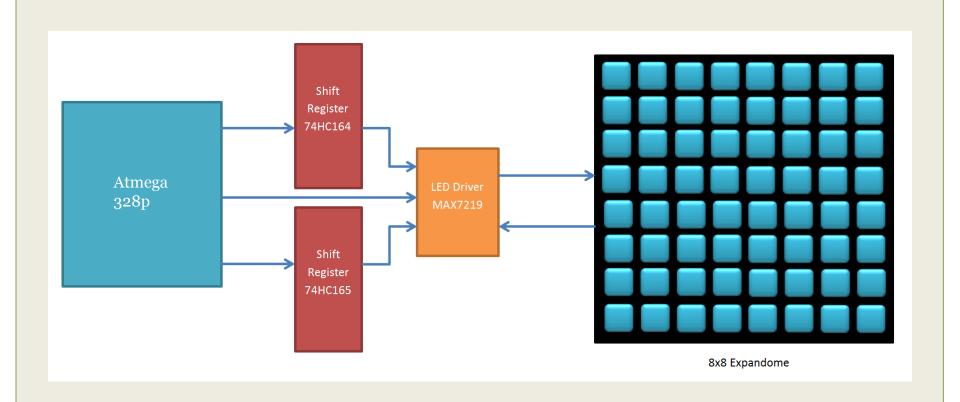


Expandome—Default Start Up

"Lights and Sounds"

The Start-Up program will perform a sequence of operations which will allow the user to verify that the following:

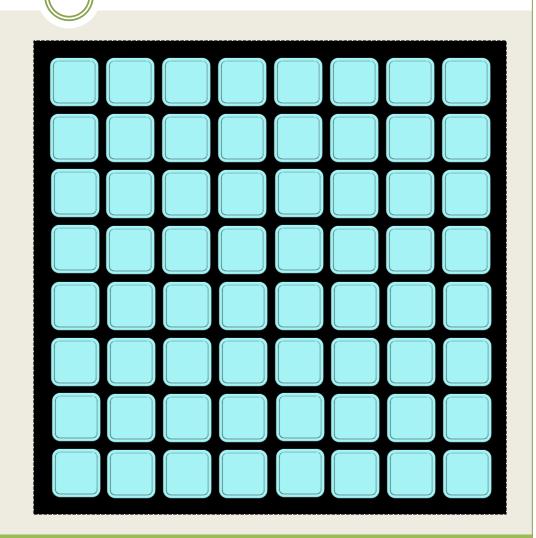- The device is connected to power
- The device has been programmed
- All LEDs are operable
- The output sound is working




Start

Expandome—Considered features

Menu


Tracks/Layers

Individual Beats

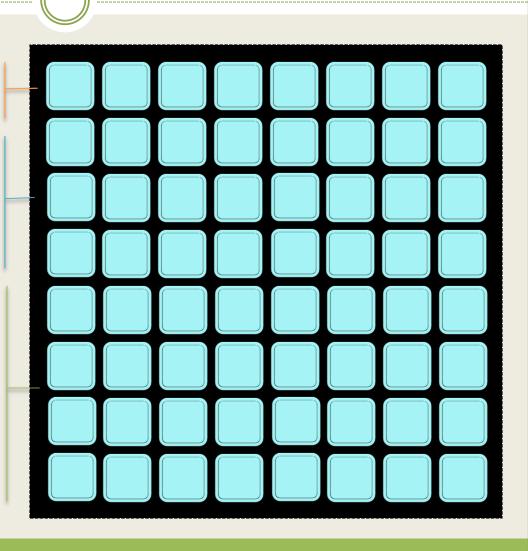

Expandome—Considered features



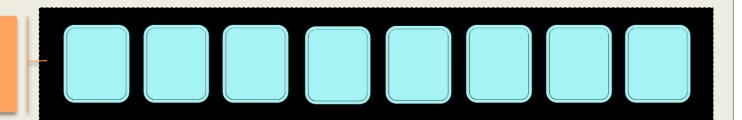


The top row of each Expandome will act as a Menu Bar with the following default settings:


- Clear All Beats
- Beat Repeat
- Clear Beat Repeat
- Track Assign*
- Record*
- Play Back*

(*This feature will not appear on the 4x4 or 4x8 devices.)


Full Implementation

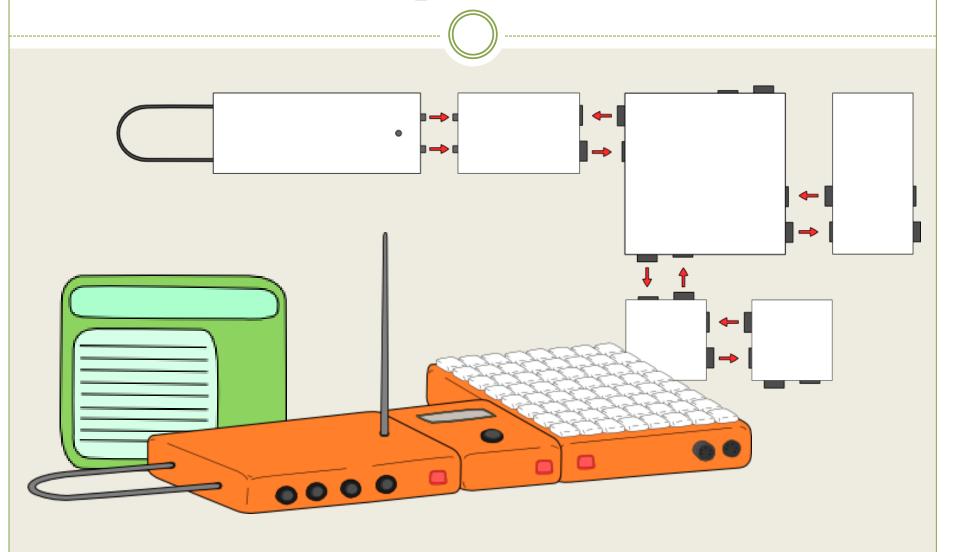

EMI Browser

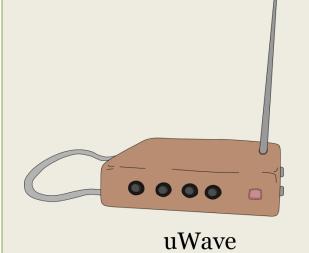



 




Expandome



EMI Browser


User Interface & Browser

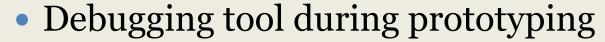


- Emulate MIDI messages
- Display communication organized by device prefixes
- Code Editor and easily integrate other coded tools

Interaction tool for regular use

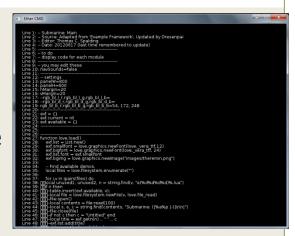- Theremin trainer
- Organize beats and button assignment
- Virtual Expandome
- SenseBox mode selection



Ether CMD

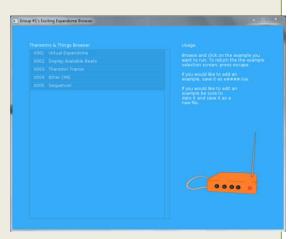

EMI Browser

Environments Explored





Beat assignment & Virtual Expandome

Theremin Trainer

Processing




o MAX/MSP



Pure Data pd~



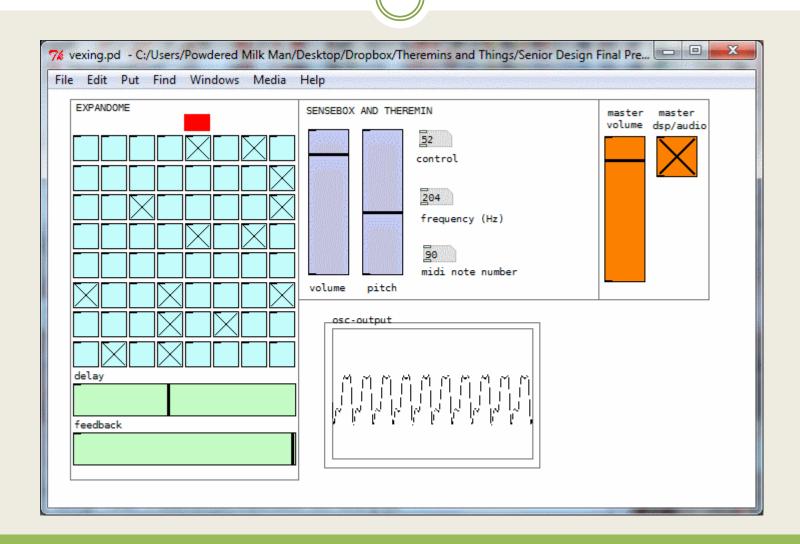

Power Requirements

uWave: +/- 12V


• 14-16VAC wall adapter in conjunction with a power supply circuit using capacitors, diodes and voltage regulators

SenseBox: 5V

• 5V via 15VDC wall adapter

Expandome 8x8 & 4x4: 5V


• 5V via USB connection to the computer

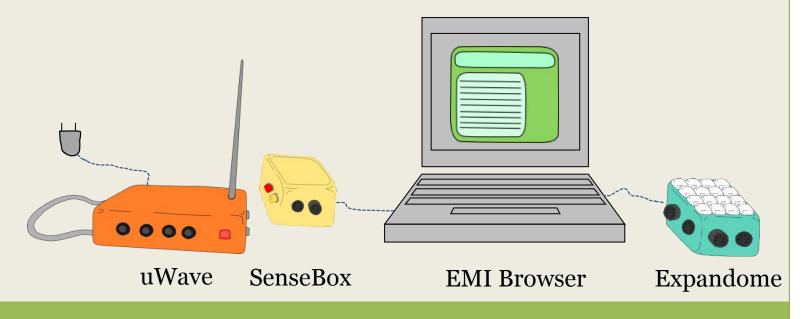


Clear Statement of Progress

- The theremin is built and operates as designed.
- The SenseBox is built and its primary functions are operating. Additional arpeggiated modes, ARP1 & ARP2 are still in beta phase.
- The 8x8 Expandome has been built, and has a myriad of available setups.
- The Expandome Browser has been made and is fully capable of routing the devices as well as as a self-contained demonstration.


Testing the uWave Theremin

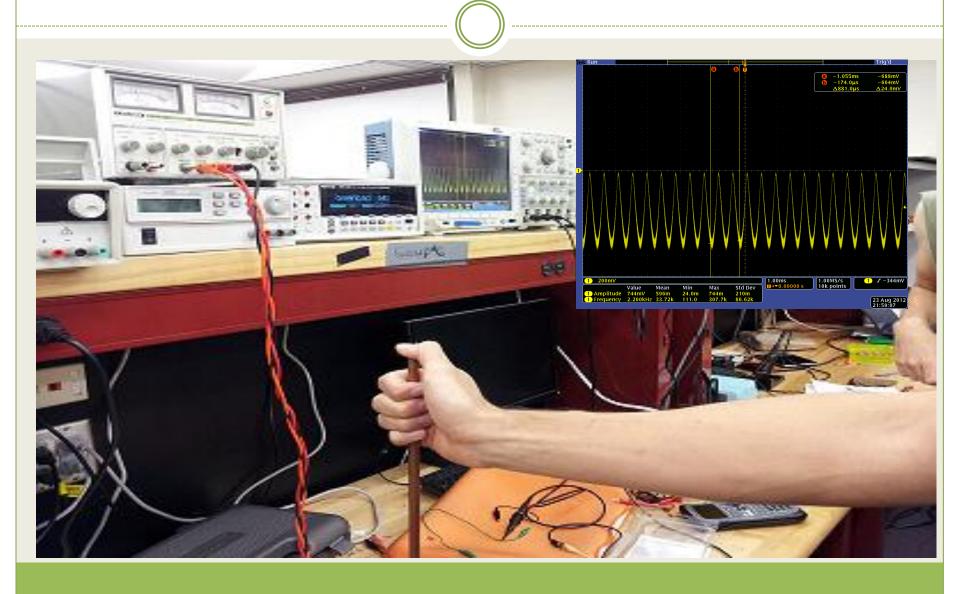


Testing the uWave Theremin

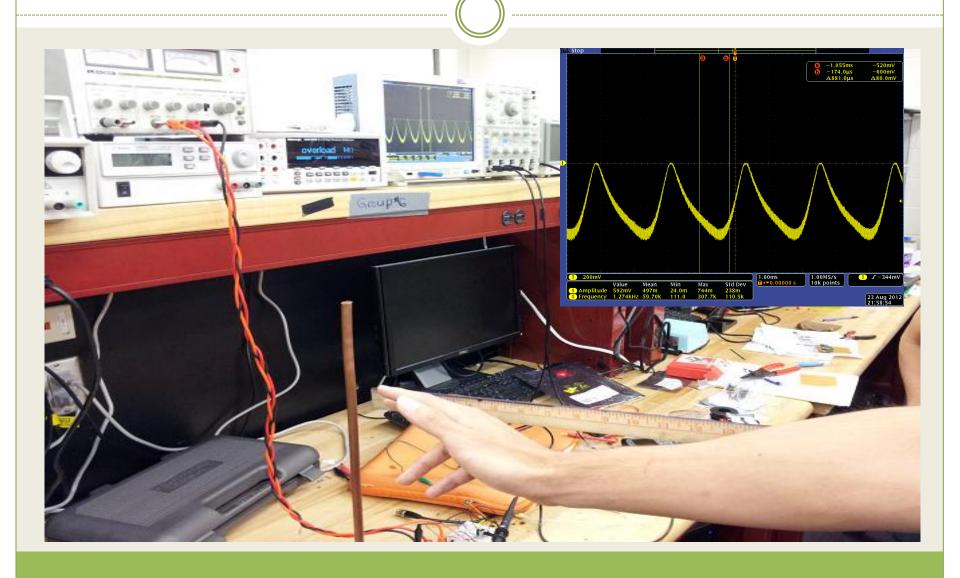


Testing the uWave Theremin

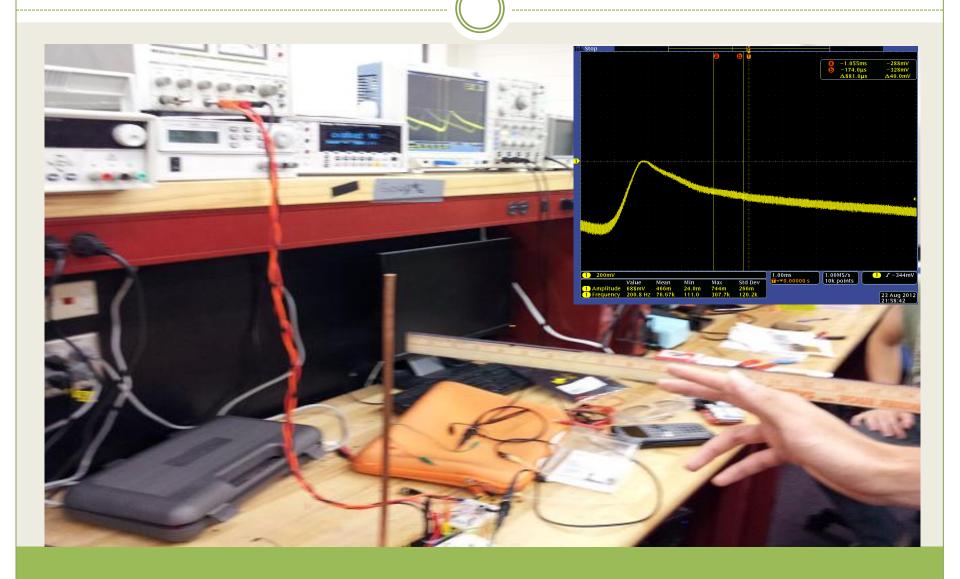

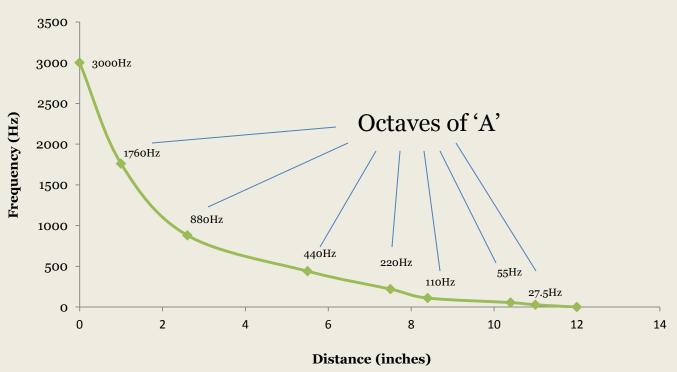uWave Theremin pitch tone versus players hand proximity




Volume Testing

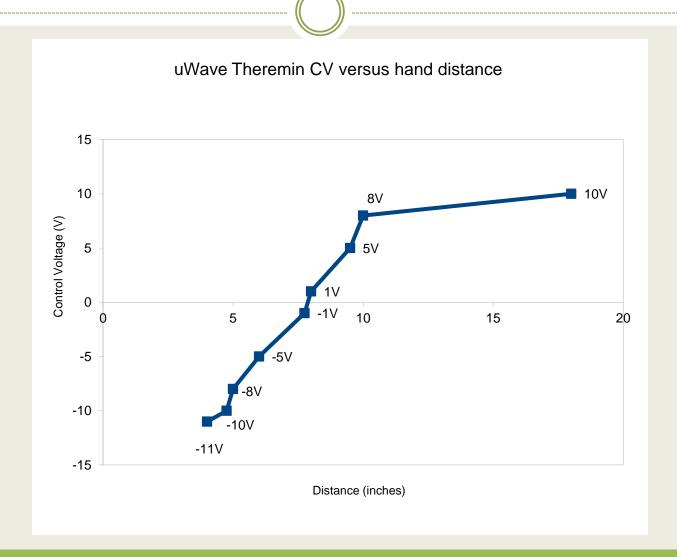

SenseBox Testing



Testing, connections, and apps

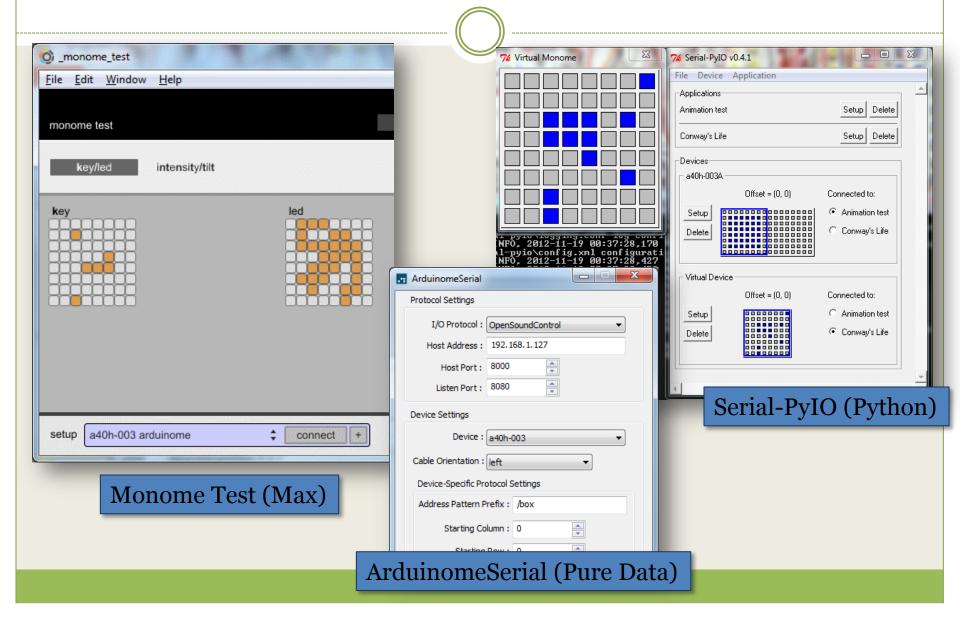

Emulation and Further Expansion w/Apps



Theremin - Difficulties

Difficulties

- Careful consideration when placing parts on PCB is needed
 - ➤ Antenna inductors must be placed 1" from each other
 - ▼ VPO and FPO should be separated by a few inches
- Controlled test environment
 - ▼ Sound Quality
 - **x** Tuning issues


SenseBox - Difficulties

Difficulties

• Had issues retrieving volume data from the uWave Theremin.

Accurately measure incoming frequency from the uWave


Theremin.

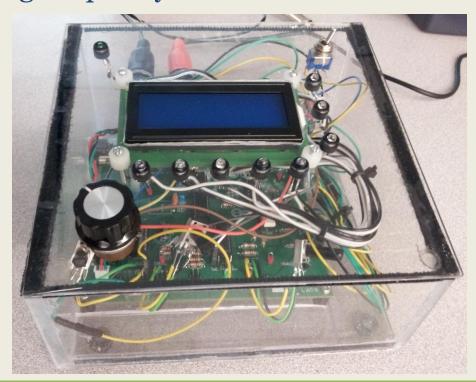

Expandome—Difficulties

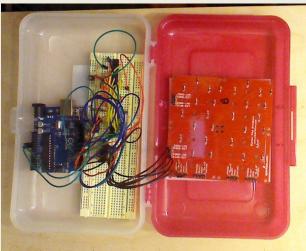- Serial protocol/communication and firmware recognition between the microprocessor and computer.
- External wiring issues








Project Budget and Financing to date and to end of project

COST ESTIMATE

Project Title:	uWave/SenseBox/Expandome	Date: <u>7/29/2012</u>			
Group: GROUP 1					
ITEM	DESCRIPTION	QTY	UNIT	UNIT COST	LINE TOTAL
1	uWave Theremin	1	each	\$ 150.00	\$ 150.00
2	Expandome 8x8	1	each	\$ 200.00	\$ 200.00
3	Expandome 4x8	1	each	\$ 150.00	\$ 150.00
4	Expandome 4x4	1	each	\$ 100.00	\$ 100.00
5	MIDI Interface	1	each	\$ 100.00	\$ 100.00
6	Power Supply	1	each	\$ 50.00	\$ 50.00
7	Software	1	each	\$ 50.00	\$ 50.00
8	Enclosure	5	each	\$ 100.00	\$ 500.00
	TOTAL ESTIMATE				\$ 1,300.00

Progress

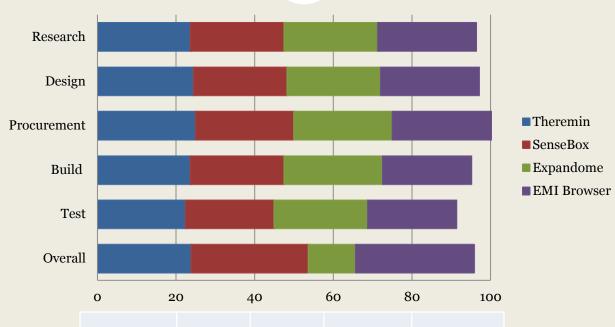

	Theremin	SenseBox	Expandome	EMI Browser
Research	95%	95%	95%	100%
Design	98%	95%	95%	100%
Procurement	100%	100%	100%	100%
Build	95%	95%	100%	90%
Test	90%	90%	95%	90%
Overall	96%	95%	97%	96%



Open question time



Thank You

